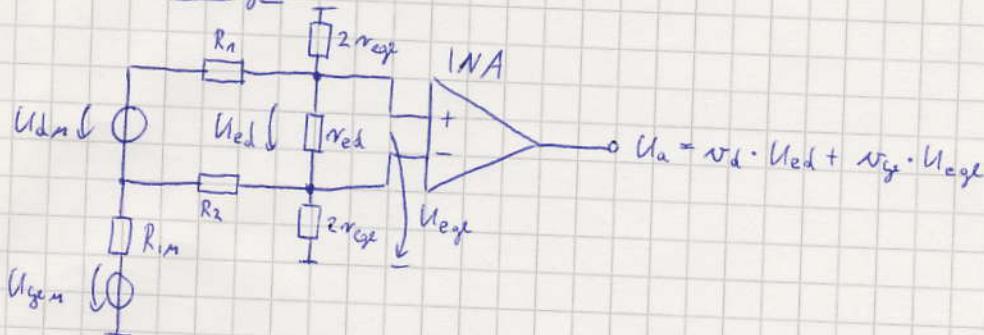


Instrumentationsverstärker

- Aufgabe:
 - Verstärkung von Differenzspannungen mit einstellbarem v
 - sehr hohe Gleichaktstabilisierung
 - sehr hoher Eingangswiderstand

Analyse



$U_{d.m.}$... Meßspannung - Nutzsignal



$U_{g.m.}$... Gleichaktspannung / Störspannung

R_{in} ... Isolatorwiderstand des Sensors (Gehäuse - Ende)

$R_{1/2}$... Leitungsleiterwiderstände, z.B. bei direktem Anschluß des Sensors:
 $R_1 = R_i(U_{d.m.})$, $R_2 \ll R_1$ ($R_2 \rightarrow 0$)

Agnish: $R_1, R_2 \ll r_{ed}, r_{ge}$ $\rightarrow U_{ed} \approx U_{d.m.}$

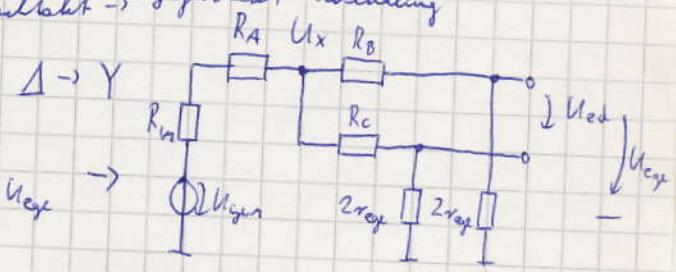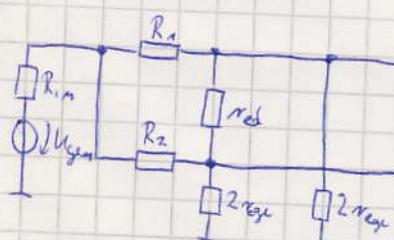Fehler durch $r_{ed}, r_{ge} \ll \infty$: \rightarrow Gleichakt-, Gegenakt-Wandlung



$$R_A = \frac{R_1 R_2}{R_1 + R_2 + r_{ed}} \approx 0$$

$$U_X = U_{g.m.} \cdot \frac{(R_0 + 2r_{reg}) || (R_C + 2r_{reg})}{R_m + (R_0 + 2r_{reg}) || (R_C + 2r_{reg})} \quad | R_A \approx 0$$

$$R_B = \frac{R_1 r_{ed}}{R_1 + R_2 + r_{ed}} \approx R_1$$

$$r_{ge} \gg R_1, R_2:$$

$$R_C = \frac{R_2 r_{ed}}{R_1 + R_2 + r_{ed}} \approx R_2$$

$$U_X = U_{g.m.} \cdot \frac{r_{ge}}{R_m + r_{ge}}$$

$$U_{ed} = U_X \left(\frac{2r_{reg}}{R_0 + 2r_{reg}} - \frac{2r_{reg}}{R_C + 2r_{reg}} \right) = U_X \left(\frac{2r_{reg}}{R_1 + 2r_{reg}} - \frac{2r_{reg}}{R_2 + 2r_{reg}} \right)$$


$$U_{ed} = U_x \frac{2r_{ge}(R_2 - R_1)}{(R_1 + 2r_{ge})(R_2 + 2r_{ge})} \approx \frac{R_2 - R_1}{2r_{ge}} \cdot U_x \quad \text{für}$$

$$U_{ed} = \frac{U_{gem}}{2} \cdot \frac{R_2 - R_1}{R_{in} + r_{ge}}$$

$$U_{ge} = \underbrace{\frac{2r_{ge}}{R_{in} + R_c + 2r_{ge}} \cdot U_{gem}}_{\text{unten Cr-Terme}} + \underbrace{\frac{U_{gem}}{4} \frac{R_2 - R_1}{R_{in} + r_{ge}}}_{\text{halbe Ueff}} \approx \frac{2r_{ge}}{R_{in} + 2r_{ge}} U_{gem}$$

$\rightarrow R_{in}, r_{ge}$ möglichst groß, $R_2 \approx R_1$

Instrumentationsverstärker mit 10 PV

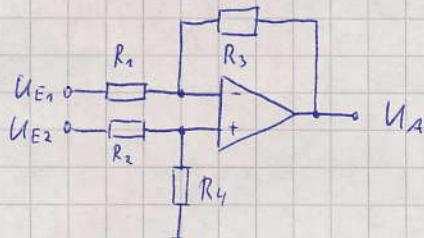

$$+: U_p = U_{E2} \cdot \frac{R_4}{R_2 + R_4}$$

$$-: U_N = U_{E1} \frac{R_3}{R_2 + R_3} + U_A \cdot \frac{R_1}{R_1 + R_3}$$

idealer OPV: $U_p = U_N$

$$U_A = \frac{R_1 + R_3}{R_1} \left(U_{E2} \frac{R_4}{R_2 + R_4} - U_{E1} \frac{R_3}{R_2 + R_3} \right) \rightarrow \text{Dimensionierung auf } U_{ge} = 0$$

$$\rightarrow \frac{R_4}{R_2 + R_4} = \frac{R_1}{R_2 + R_3}$$

$$\rightarrow U_A = \underbrace{\frac{R_3}{R_1}}_{v_d} \underbrace{\left(U_{E2} - U_{E1} \right)}_{U_d}$$

$$\rightarrow R_2 + R_3 = R_2 + R_4$$

$$\rightarrow R_1 = R_2, R_3 = R_4$$

$$v_{ge, \text{ideal}} = 0$$

Gleichaktuntendrückung, real ($A_{ge} = \infty$ -Gleichaktuntendrückung)

$$R_i = R_{io} \cdot (1 \pm \delta) \quad i = 1 \dots 4 \quad G_{ov} = \frac{v_d}{v_{ge}} = CMR$$

Fehler durch v_{ge} :

$$U_{ge} = U_{ge} \cdot \frac{R_4}{R_2 + R_4}$$

$$U_{A,v_d} = U_{ge} \cdot v_{ge} \cdot \frac{R_1}{R_2 + R_4}$$

$$\left(\frac{v_{ge}}{G_{ov}} = \frac{|v_d|}{1 + |v_d|} + \frac{1}{1 + |v_d|} \delta \right) \approx \text{worst case für alle 4 R}$$

$$G = \frac{1}{\frac{1}{G_{ov}} + \frac{46}{|v_d'| + 1}}$$

Bsp. $G = 0,1\%$

$$|v_d'| = 1 \Rightarrow G = 500 \hat{=} 54 \text{ dB}$$

$$G_{ov} = 120 \text{ dB} = 10^6$$

→ 4 hochgenaue R notwendig zur Gleichaktunterscheidung

- weitere Nachteile: - rege und res klein

- zur Änderung von v' sind 2 Rs zu ändern

3.oops Common Mode Input Range


$$U_+ = U_{ge} \frac{R_4}{R_2 + R_4} = U_-$$


$$\underline{U_{+max}} = U_{ge,max} = U_{+max} \left(1 + \frac{R_2}{R_4} \right) = U_{+max} \left(1 + \frac{1}{v'} \right)$$

für $v' \gg 1$ wird der Gleichaktbereich nicht vergrößert

Tafel INA 105

Erhöhung des Eingangswiderstandes durch OPV als Spannungsfolger

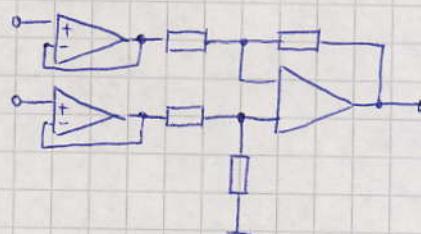

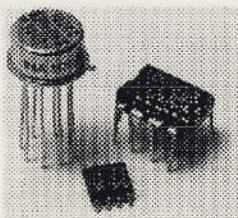

INA105

Precision Unity Gain DIFFERENTIAL AMPLIFIER

FEATURES

- CMR 86dB min OVER TEMPERATURE
- GAIN ERROR: 0.01% max
- NONLINEARITY: 0.001% max
- NO EXTERNAL ADJUSTMENTS REQUIRED
- EASY TO USE
- COMPLETE SOLUTION
- HIGHLY VERSATILE
- LOW COST
- PLASTIC DIP, TO-99 HERMETIC METAL, AND SO-8 SOIC PACKAGES


APPLICATIONS

- DIFFERENTIAL AMPLIFIER
- INSTRUMENTATION AMPLIFIER BUILDING BLOCK
- UNITY-GAIN INVERTING AMPLIFIER
- GAIN-OF-1/2 AMPLIFIER
- NONINVERTING GAIN-OF-2 AMPLIFIER
- AVERAGE VALUE AMPLIFIER
- ABSOLUTE VALUE AMPLIFIER
- SUMMING AMPLIFIER
- SYNCHRONOUS DEMODULATOR
- CURRENT RECEIVER WITH COMPLIANCE TO RAILS
- 4mA TO 20mA TRANSMITTER
- VOLTAGE-CONTROLLED CURRENT SOURCE
- ALL-PASS FILTERS

DESCRIPTION


The INA105 is a monolithic Gain = 1 differential amplifier consisting of a precision op amp and on-chip metal film resistors. The resistors are laser trimmed for accurate gain and high common-mode rejection. Excellent TCR tracking of the resistors maintains gain accuracy and common-mode rejection over temperature.

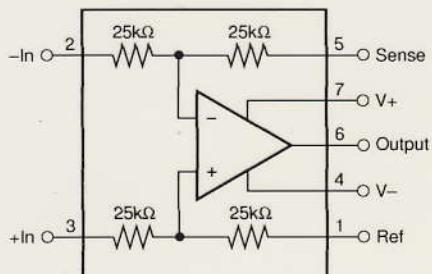The differential amplifier is the foundation of many commonly used circuits. The INA105 provides this precision circuit function without using an expensive precision resistor network. The INA105 is available in 8-pin plastic DIP, SO-8 surface-mount and TO-99 metal packages.



International Airport Industrial Park • Mailing Address: PO Box 11400, Tucson, AZ 85734 • Street Address: 6730 S. Tucson Blvd., Tucson, AZ 85706 • Tel: (520) 746-1111 • Twx: 910-952-1111
Internet: <http://www.burr-brown.com/> • FAXLine: (800) 548-6133 (US/Canada Only) • Cable: BBRCORP • Telex: 066-6491 • FAX: (520) 889-1510 • Immediate Product Info: (800) 548-6132

2-OPV Instrumenteneinverstärker

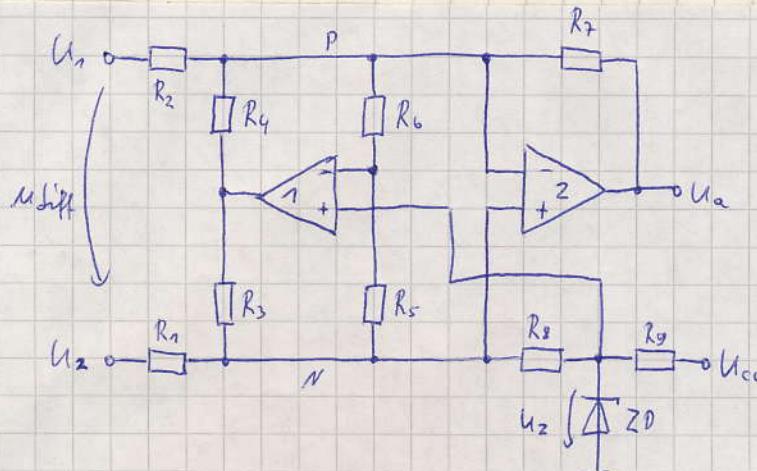

- U_2 wird in die Mitte der Versorgungsspannungen gelegt
- $U_{\text{diff}} = 0 \rightarrow \mathcal{D}_{R5}, \mathcal{D}_{R6} = 0, U_{\text{diff}} = 0$
 $U_+ = U_- = U_2$ für beide OPV

für $U_1 = U_2 = U_2 \rightarrow \mathcal{D}_{R1} = \mathcal{D}_{R2} = 0 \rightarrow \mathcal{D}_{R7} = 0, U_a = U_2$

- Gleichakt - Eingangsspannung:

$$\begin{aligned} \mathcal{D}_{R1} &= \mathcal{D}_{R2} & \text{OPV1 stellt den Gleichakt } U_p = U_N \text{ auf } U_2 \\ &= \mathcal{D}_{R3} = \mathcal{D}_{R4} \end{aligned}$$

$$r_{\text{geg}} = R_1 \| R_2$$

- Differenzaussteuerung

$$U_{\text{diff}} = 0 \text{ wegen OPV2 } (U_p = U_N)$$

$$r_{\text{diff}} = \frac{U_{\text{diff}}}{R_1 + R_2} \Rightarrow r_{\text{diff}} = R_1 + R_2$$

$$\text{wegen } U_1 = U_2 \rightarrow U_{R8} = 0, \mathcal{D}_{R8} = 0$$

$$\mathcal{D}_{R1} = \mathcal{D}_{R3}, \mathcal{D}_{R5} = \mathcal{D}_{R6} = 0$$


$$\mathcal{D}_{R7} = \mathcal{D}_{R4} + \mathcal{D}_{R2} = 2\mathcal{D}_{R4}$$

$$\Rightarrow U_a = U_2 - \frac{2R_7}{R_1 + R_2} \cdot U_{\text{diff}}$$

- Nur noch R_7 zur Verstärkungseinstellung zu ändern

- anderen Maßstabe bleiben

3 - OPV Instrumentationsverstärker

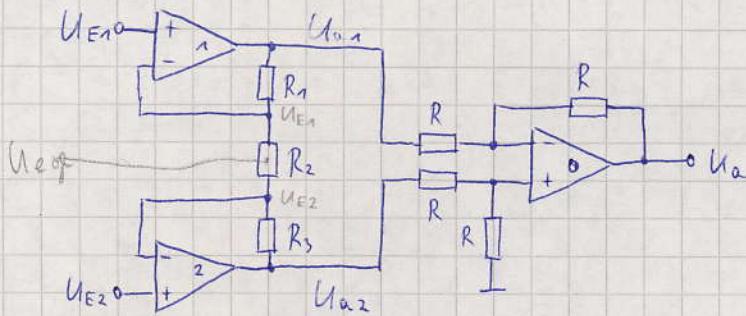

ideale OPV:

$$N_d' = \frac{U_{a1} - U_{a2}}{U_{E1} - U_{E2}}$$

Querstrom

$$\frac{U_{a1} - U_{a2}}{R_1 + R_2 + R_3} = \frac{U_{E1} - U_{E2}}{R_2} \rightarrow N_d' = \frac{R_1 + R_2 + R_3}{R_2} = 1 + \frac{R_1 + R_3}{R_2}$$

Gleichaktverstärkung:

$$U_{E1} = U_{E2} = U_{Ege}, \text{ wegen } U_d = 0 \rightarrow D_{R2} = 0 \rightarrow U_{a1} = U_{a2} = U_{Ege}$$

$$N_d' \text{ in. Stufe} = 1$$

$$N_d' \text{ ges} = N_d' \text{ in. Stufe} \cdot N_d' \text{ o. Stufe}$$

Gleichaktstundruckung:

$$G' = \frac{N_d'}{N_d'_{\text{in}}} = N_d' = 1 + \frac{R_1 + R_3}{R_2} \quad \text{erste Stufe}$$

$$G_{\text{ges}} = \frac{N_d' \text{ ges}}{N_d' \text{ ges}} = G' G_o = N_d' G_o \quad \text{gesamt}$$

Nichtideale OPV

$$\frac{U_{a1} - U_{a2}}{U_{Ege}} = \frac{U_{ad}}{U_{Ege}} \approx N_d' \left(\frac{1}{G_1} - \frac{1}{G_2} \right)$$

- ohne Ablesung

- Gleichakt-Gegentakt-Konversion
- für $G_1 = G_2 \rightarrow U_{ad} = 0$, keine Gleichakt-Gegentakt-Konversion

$$N_d' \text{ ges} = N_{d,0} \cdot 1 + N_{d,0} \cdot N_d' \left(\frac{1}{G_1} - \frac{1}{G_2} \right) \quad N_{d,0} = A$$

$$G_{\text{ges}} = \frac{N_d'}{N_{d,0} + N_d' \left(\frac{1}{G_1} - \frac{1}{G_2} \right)} = \frac{N_d' G_o}{1 + G_o N_d' \left(\frac{1}{G_1} + \frac{1}{G_2} \right)}$$

Tabelle PGA 204


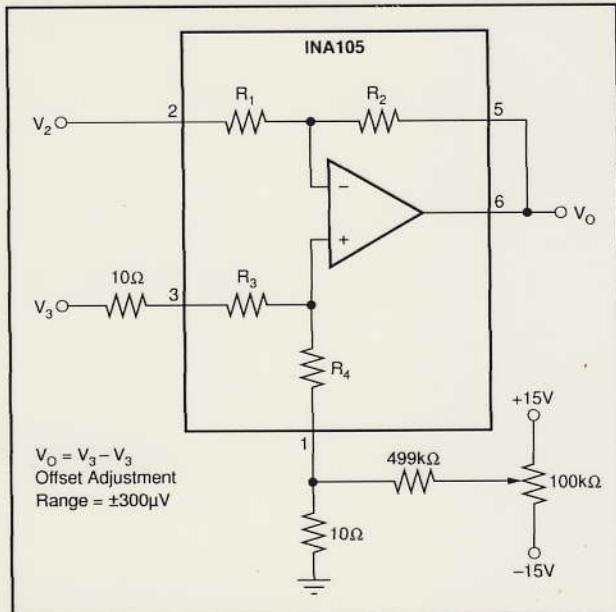


FIGURE 2. Offset Adjustment.

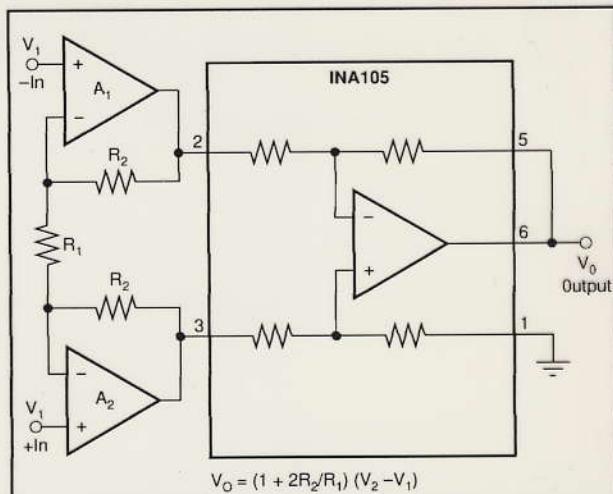

For low source impedance applications, an input stage using OPA27 op amps will give the best low noise, offset, and temperature drift performance. At source impedances above about $10\text{k}\Omega$, the bias current noise of the OPA27 reacting with the input impedance begins to dominate the noise performance. For these applications, using the OPA11 or dual OPA2111 FET input op amp will provide lower noise performance. For lower cost use the OPA121 plastic. To construct an electrometer use the OPA128.

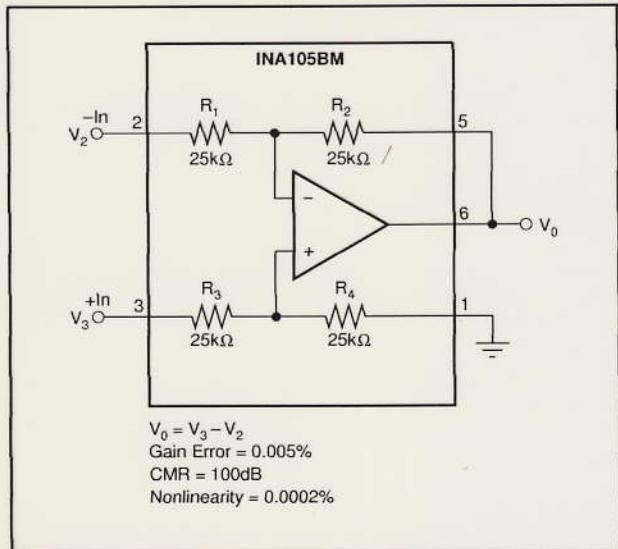


FIGURE 3. Precision Difference Amplifier.

A ₁ , A ₂	R ₁ (Ω)	R ₂ (Ω)	GAIN (V/V)	CMRR (dB)	MAX I _B	NOISE AT 1kHz (nV/√Hz)
OPA27A	50.5	2.5k	100	128	40nA	4
OPA111B	202	10k	100	110	1pA	10
OPA128LM	202	10k	100	118	75fA	38

FIGURE 4. Precision Instrumentation Amplifier.


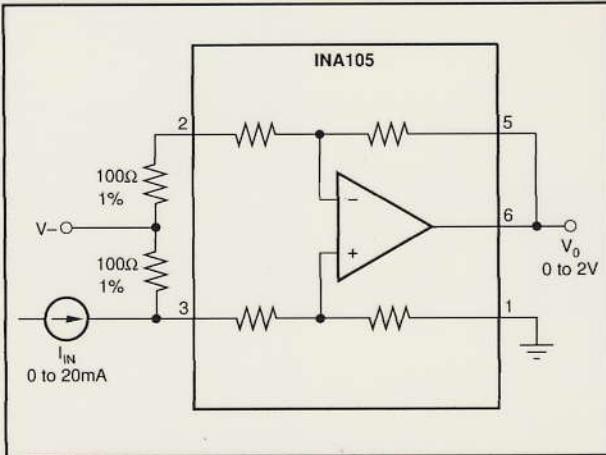


FIGURE 5. Current Receiver with Compliance to Rails.

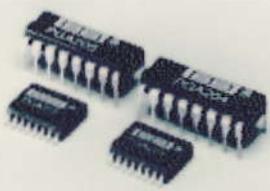

PGA204
PGA205

Programmable Gain INSTRUMENTATION AMPLIFIER

FEATURES

- DIGITALLY PROGRAMMABLE GAIN:
PGA204: G=1, 10, 100, 1000V/V
PGA205: G=1, 2, 4, 8V/V
 - LOW OFFSET VOLTAGE: $50\mu\text{V}$ max
 - LOW OFFSET VOLTAGE DRIFT: $0.25\mu\text{V}/^\circ\text{C}$
 - LOW INPUT BIAS CURRENT: 2nA max
 - LOW QUIESCENT CURRENT: 5.2mA typ
 - NO LOGIC SUPPLY REQUIRED
 - 16-PIN PLASTIC DIP, SOL-16 PACKAGES

APPLICATIONS

- DATA ACQUISITION SYSTEM
 - GENERAL PURPOSE ANALOG BOARDS
 - MEDICAL INSTRUMENTATION


DESCRIPTION

The PGA204 and PGA205 are low cost, general purpose programmable-gain instrumentation amplifiers offering excellent accuracy. Gains are digitally selected: PGA204—1, 10, 100, 1000, and PGA205—1, 2, 4, 8V/V. The precision and versatility, and low cost of the PGA204 and PGA205 make them ideal for a wide range of applications.

Gain is selected by two TTL or CMOS-compatible address lines, A₀ and A₁. Internal input protection can withstand up to $\pm 40\text{V}$ on the analog inputs without damage.

The PGA204 and PGA205 are laser trimmed for very low offset voltage ($50\mu\text{V}$), drift ($0.25\mu\text{V}/^\circ\text{C}$) and high common-mode rejection (115dB at $G=1000$). They operate with power supplies as low as $\pm 4.5\text{V}$, allowing use in battery operated systems. Quiescent current is 5mA.

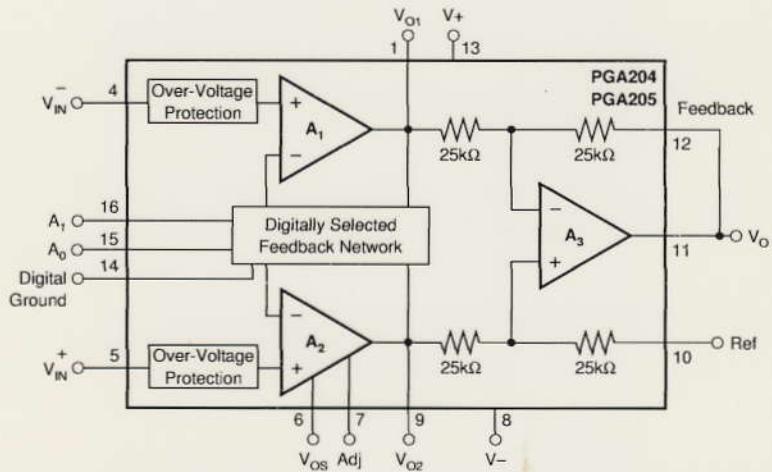The PGA204 and PGA205 are available in 16-pin plastic DIP, and SOL-16 surface-mount packages, specified for the -40°C to +85°C temperature range.



International Airport Industrial Park • Mailing Address: PO Box 11400 • Tucson, AZ 85734 • Street Address: 6730 S. Tucson Blvd. • Tucson, AZ 85706
Tel: (520) 746-1111 • Twx: 910-952-1111 • Cable: BBRCORP • Telex: 066-6491 • FAX: (520) 889-1510 • Immediate Product Info: (800) 548-6132

SPECIFICATIONS

ELECTRICAL

At $T_A = +25^\circ\text{C}$, $V_S = \pm 15\text{V}$, and $R_L = 2\text{k}\Omega$ unless otherwise noted.

PGA204 G=1, 10, 100, 1000V/V

PARAMETER	CONDITIONS	PGA204BP, BU			PGA204AP, AU			UNITS
		MIN	TYP	MAX	MIN	TYP	MAX	
INPUT								
Offset Voltage, RTI vs Temperature	$T_A=+25^\circ\text{C}$		$\pm 10+20/\text{G}$	$\pm 50+100/\text{G}$		$\pm 25+30/\text{G}$	$\pm 125+500/\text{G}$	μV
vs Power Supply	$T_A=T_{\text{MIN}} \text{ to } T_{\text{MAX}}$		$\pm 0.1+0.5/\text{G}$	$\pm 0.25+5/\text{G}$		$\pm 0.25+5/\text{G}$	$\pm 1+10/\text{G}$	$\mu\text{V}^\circ\text{C}$
Long-Term Stability	$V_S=\pm 4.5\text{V} \text{ to } \pm 18\text{V}$		$0.5+2/\text{G}$	$3+10/\text{G}$				$\mu\text{V}/\text{V}$
Impedance, Differential			$\pm 0.2+0.5/\text{G}$					$\mu\text{V}/\text{mo}$
Common-Mode			$10^{10}\ \text{G}$					$\Omega \parallel \text{pF}$
Input Common-Mode Range	$V_O=0\text{V}$ (see text)	± 10.5	$10^{10}\ \text{G}$		*	*		$\Omega \parallel \text{pF}$
Safe Input Voltage			± 12.7		± 40			V
Common-Mode Rejection	$V_{CM}=\pm 10\text{V}$, $\Delta R_S=1\text{k}\Omega$							V
	$G=1$	80	99		75	90		dB
	$G=10$	96	114		90	106		dB
	$G=100$	110	123		106	110		dB
	$G=1000$	115	123		106	110		dB
BIAS CURRENT								
vs Temperature			± 0.5	± 2				nA
Offset Current			± 8					pA°C
vs Temperature			± 0.5	± 2				nA
			± 8					pA°C
NOISE, Voltage, RTI⁽¹⁾: $f=10\text{Hz}$	$G\geq 100$, $R_S=0\Omega$		16					$\text{nV}/\sqrt{\text{Hz}}$
	$f=100\text{Hz}$		13					$\text{nV}/\sqrt{\text{Hz}}$
	$f=1\text{kHz}$		13					$\text{nV}/\sqrt{\text{Hz}}$
	$f_B=0.1\text{Hz} \text{ to } 10\text{Hz}$		0.4					$\mu\text{V}_\text{p-p}$
Noise Current								
$f=10\text{Hz}$			0.4					$\text{pA}/\sqrt{\text{Hz}}$
$f=1\text{kHz}$			0.2					$\text{pA}/\sqrt{\text{Hz}}$
$f_B=0.1\text{Hz} \text{ to } 10\text{Hz}$			18					pAp-p
GAIN, Error								
$G=1$			± 0.005	± 0.024				$\%$
$G=10$			± 0.01	± 0.024				$\%$
$G=100$			± 0.01	± 0.024				$\%$
$G=1000$			± 0.02	± 0.05				$\%$
Gain vs Temperature	$G=1 \text{ to } 1000$			± 2.5	± 10			ppm°C
Nonlinearity	$G=1$		± 0.0004	± 0.001				$\% \text{ of FSR}$
	$G=10$		± 0.0004	± 0.002				$\% \text{ of FSR}$
	$G=100$		± 0.0004	± 0.002				$\% \text{ of FSR}$
	$G=1000$		± 0.0008	± 0.01				$\% \text{ of FSR}$
OUTPUT								
Voltage, Positive ⁽²⁾	$I_O=5\text{mA}$, $T_{\text{MIN}} \text{ to } T_{\text{MAX}}$	$(V_+)-1.5$	$(V_+)-1.3$		*	*		V
Negative ⁽²⁾		$I_O=-5\text{mA}$, $T_{\text{MIN}} \text{ to } T_{\text{MAX}}$	$(V_-)+1.5$	$(V_-)+1.3$				V
Load Capacitance Stability				1000				pF
Short Circuit Current				+23/-17				mA
FREQUENCY RESPONSE								
Bandwidth, -3dB	$G=1$		1					MHz
	$G=10$		80					kHz
	$G=100$		10					kHz
	$G=1000$		1					kHz
Slew Rate	$V_O=\pm 10\text{V}$, $G=10$	0.3	0.7		*	*		$\text{V}/\mu\text{s}$
Settling Time ⁽³⁾ , 0.1%	$G=1$		22					μs
	$G=10$		23					μs
	$G=100$		100					μs
	$G=1000$		1000					μs
0.01%	$G=1$		23					μs
	$G=10$		28					μs
	$G=100$		140					μs
	$G=1000$		1300					μs
Overload Recovery	50% Overdrive		70					μs
DIGITAL LOGIC								
Digital Ground Voltage, V_{DG}		V_-		$(V_+)-4$				V
Digital Low Voltage		V_-		$V_{DG}+0.8\text{V}$				V
Digital Input Current			1					μA
Digital High Voltage		$V_{DG}+2$		V_+				V
POWER SUPPLY , Voltage								
Current	$V_{IN}=0\text{V}$	± 4.5	± 15	± 18	*	*		V
			+5.2/-4.2	± 6.5				mA
TEMPERATURE RANGE								
Specification		-40		$+85$				$^\circ\text{C}$
Operating		-40		$+125$				$^\circ\text{C}$
θ_{JA}			80					$^\circ\text{C/W}$

* Specification same as PGA204BP.

NOTES: (1) Input-referred noise voltage varies with gain. See typical curves. (2) Output voltage swing is tested for $\pm 10\text{V}$ min on $\pm 11.4\text{V}$ power supplies. (3) Includes time to switch to a new gain.

